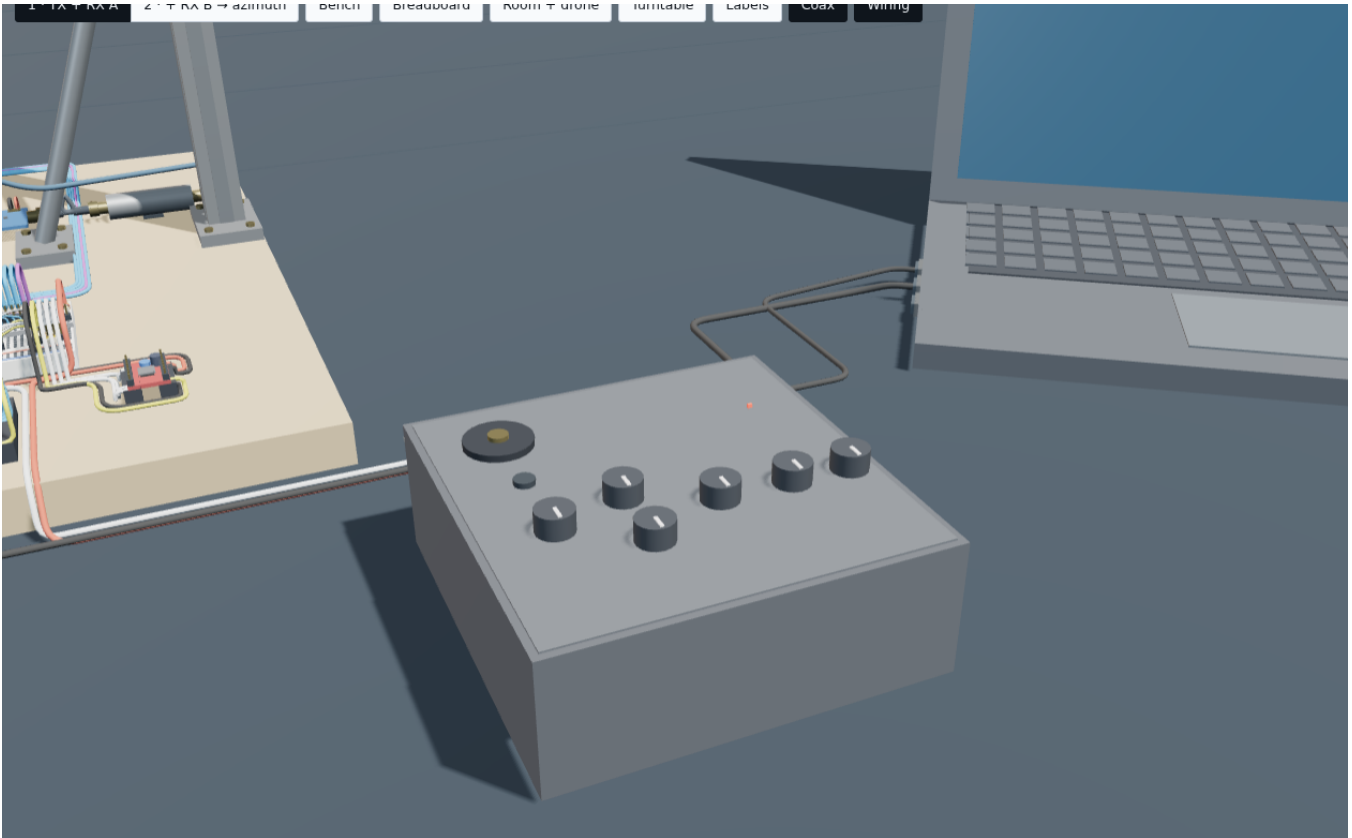


Assembly and bring-up

How it all goes together, and how to prove each stage works



The bench in use, from the 3-D model: horns on the frame, RF chain along the front of the board, the breadboard behind it, the sound card and laptop alongside.

Part 1 (fabrication) has the parts list, the copper templates, the frame drawings and the schematics. This part assumes you have the parts in hand and the pieces cut.

Work in the order of the stages. Each one ends with a **gate**: a measurement that must pass before you go on. A fault found at its own gate takes minutes; the same fault found at the end takes an evening.

Conventions

- sizes in millimetres
- “left” and “right” are as you sit behind the bench, the horns pointing away from you into the room; “front” is the horn side
- SWEEP 1 is something you type into the ESP32’s serial monitor
- numbers like R4, C9, J12 match the schematics and the breadboard

Contents

1 The order of work	3
2 Stage 2: the three horns	4
3 Stage 3: the frame	9
4 Stage 4: the breadboard	11
5 Stage 5: power	26
6 Stage 6: firmware and software	27
7 Stage 7: mount and cable	29
8 Stages 8 to 10: bring-up	31
9 When something is wrong	33

1 The order of work

Three jobs can run side by side while parts are arriving: the horns, the frame, and the breadboard. Everything after that is in series. The horns are the longest job; start them first.

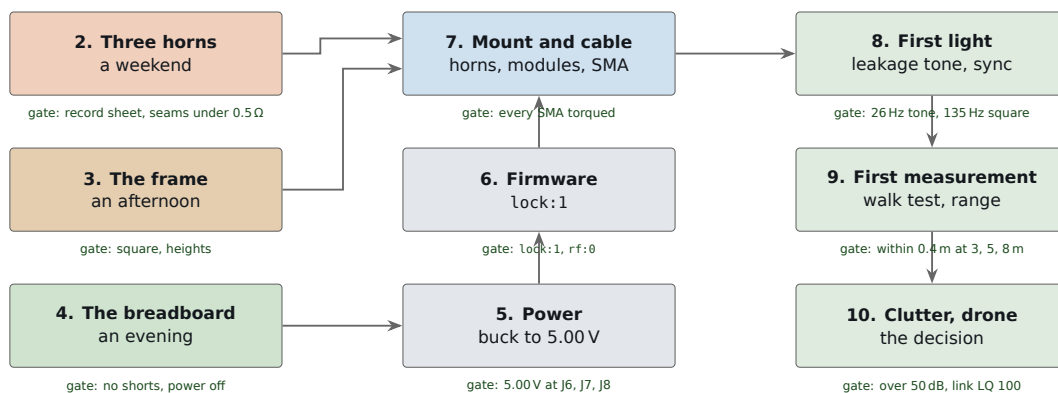


Figure 1: The build in stages. Stages 2, 3 and 4 can be done in any order or at the same time; from stage 5 on, each needs the one before it.

	stage	what you end up with	the gate
2	Three horns	three identical copper horns with connectors	each passes the record sheet
3	The frame	plywood board, uprights, beams, saddles	square, beam tops at 252.8 and 542.8
4	The breadboard	the amplifier and power board, fully wired	no shorts between rails, power off
5	Power	5.00 V to each module header, 12 V to the op-amps	rail voltages in the table on page 26
6	Firmware	the ESP32 talking to the PLL	lock:1 with RF off
7	Mount and cable	everything in place and connected	every SMA done up, still unpowered
8	First light	the transmitter heard leaking into the receiver	a low tone with a 26 Hz part; a 135 Hz square wave
9	First measurement	a person tracked across the room	range within 0.4 m at 3, 5 and 8 m
10	Clutter and drone	the number that decides what the radar can see	clutter cancellation over 50 dB

2 Stage 2: the three horns

Make all three at once, step by step: cut all three sets, then fold all three, and so on. You get faster with every piece, and the two receive horns come out as twins, which matters later. Use the full-size templates in part 1.

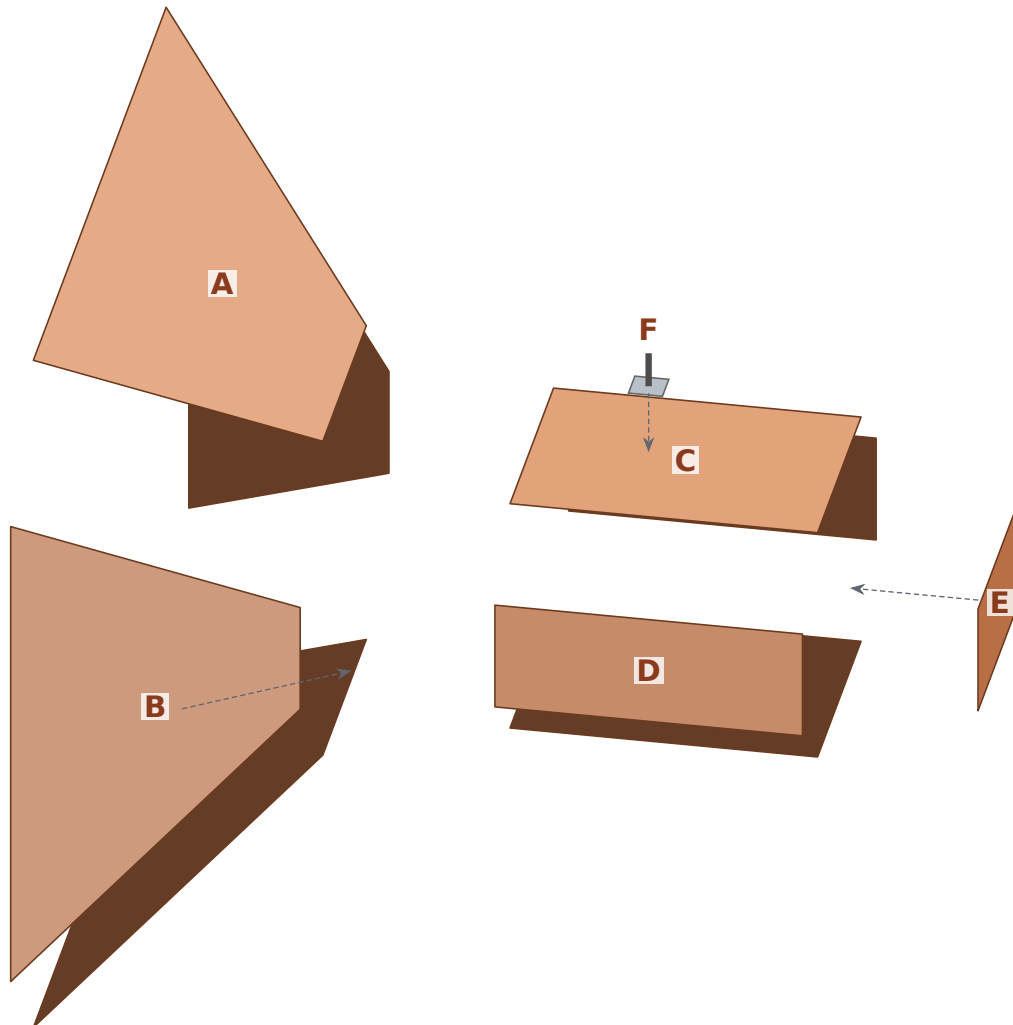


Figure 2: How the nine pieces and the connector go together. The pipe comes first (C, D, E), then the connector (F), then the flare (A, B) on the collar formed by the pipe's front tabs.

1 Mark, cut and deburr

On a waterjet

Cut the three sheets from `build/waterjet/horn_sheet_mm.dxf` as its README says, then skip to item 3 below: deburr and flatten. The feed hole in C is already cut, so step 2 is only the four flange holes.

1. Tape the paper templates to the copper, outside face up, and scribe round them. Write each piece's letter on its outside face.
2. Cut with the snips, blade just outside the line. Cut the angled ends of the B tabs and the notched corners of E last.
3. File every edge smooth and flatten any piece the snips curled: lay it flat and press it with a block of wood.

Check. every piece against its size in part 1, with calipers. A within 1 mm on both parallel edges; both slanted edges of A and B 147.9 within 1 mm.


2 Drill the feed hole while the top wall is flat

1. On *one* C only, mark a point 43.7 up from the back edge and halfway across ($87.5/2$ from either side). Centre-punch it.
2. Drill a small pilot, then open it to 4.5 mm so it clears the connector's white insulator. Deburr both sides.
3. Hold the SMA flange over the hole, centred and square to the edges, and mark its four holes through it. Drill them 2.7 mm.

Check. the flange sits flat over the hole with its four screws through, and the centre pin is in the middle of the hole.

3 Fold the tabs

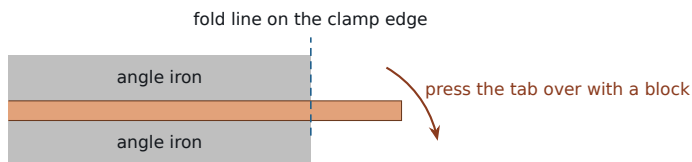Clamp the piece between two straight edges (angle iron or hardwood) with the fold line exactly on their edge, then press the tab over with a block of wood. Never fold by hand: it rounds the corner.



which way each tab goes

C side tabs, E tabs, B tabs: **away** from the outside face, so they wrap round the neighbouring wall.
C and D front tabs: **towards** the outside face, flaring out like a funnel rim. That rim is the collar.

piece	fold to	how to set it
C side tabs, E tabs	90°	square against the clamp
B slanted-edge tabs	64°	a card gauge cut to 64°; they lap over A at the corners
C front tabs	39° out	the card gauge on page 7; set later, at step 7
D front tabs	44° out	the card gauge on page 7; set later, at step 7

4 Build the pipe

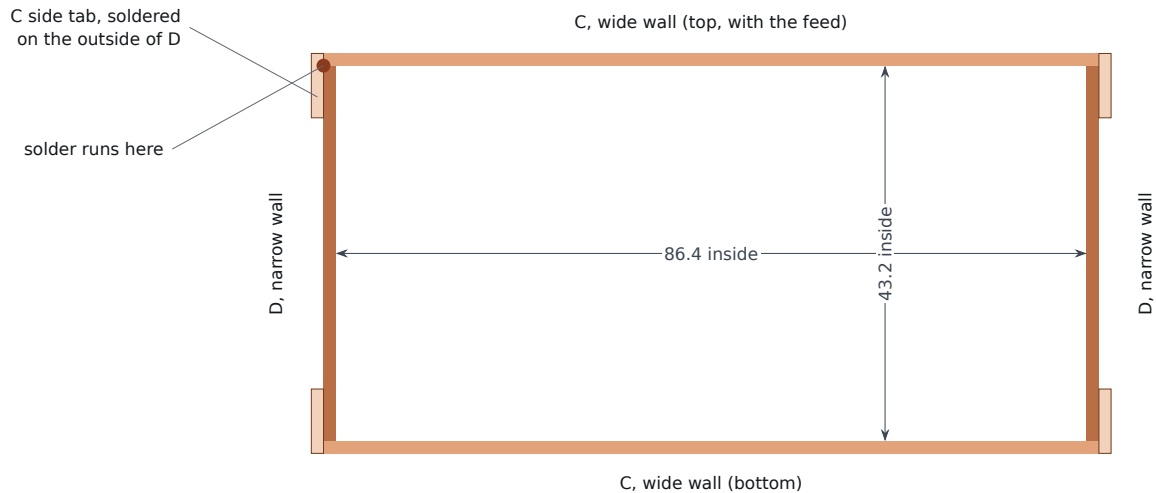


Figure 3: Looking into the pipe from the front, copper thickness exaggerated. The wide walls lap over the edges of the narrow ones; that is why C is cut 87.5, a little over 86.4.

1. Stand the two D walls on edge, 86.4 apart inside, and lay the bottom C across them with its side tabs folded down over their outsides. Clamp.
2. Turn the box over and fit the top C, feed hole up, the same way.
3. Measure inside at both ends with calipers: 86.4×43.2 , within half a millimetre, and the two diagonals equal. Adjust before any solder goes on.
4. Tack each corner with a spot of solder, check again, then run solder along every tab from the outside. Keep the inside clean: solder blobs inside change the pipe's size.

5 Close the back

Slide the back wall E over the back of the pipe, tabs forward over the outside, and solder all four tabs. The inside face of E is what the probe position is measured from, so it must sit flat and square across the whole end.

Check. inside, from the face of E to the centre of the feed hole: 43.7 ± 0.5 .

6 Fit the connector and the probe

1. Cut 32 of brass rod and solder one end into the connector's centre cup, straight in line with it. If the rod will not enter the cup, file its end down until it does.
2. Scrape the copper bright around the hole. Push the rod in through the hole and bolt the flange down tight with M2.5 screws: it must touch bare copper all round.
3. Trim the rod so 28 stands inside, measured from the inside face of the wall. It must hang straight, square to the wall.

The probe is the one part worth tuning

Its length and its distance from the back wall decide how much signal goes into the horn instead of bouncing back down the cable. If the HFSS model settles on different numbers, use those. To trim later, unbolt the connector and lift it out with the rod attached.

7 Add the flare

1. Set the collar with the card gauges (page 7): the two C front tabs lean out 39°, the two D front tabs 44°.
2. Set the top and bottom panels (A) on the C collar tabs, short edge to the pipe. Tack each at the middle of its short edge only.
3. Set the side panels (B) on the D collar tabs, their slanted tabs over the outside of the A panels. Tack each at its short edge.
4. Pull the corners together and tack each corner seam at the mouth.
5. Measure the mouth at the rim: 263.8 × 193.1 inside, diagonals equal. Squeeze or spread the corners until it is, then tack the middle of each corner seam.
6. Run the four corner seams and the collar, all from the outside, working from the pipe towards the mouth.

8 Check it, and fill in the record


With a multimeter on its lowest resistance range, check every seam piece to piece, the connector body to the copper, and the centre pin to the copper. Then measure everything below.

check	target	horn 1 (TX)	horn 2 (RX)	horn 3 (spare RX)
mouth width, inside	263.8 ± 2			
mouth height, inside	193.1 ± 2			
mouth diagonals	equal ± 2			
flare depth, mouth to pipe	91.5 ± 1			
pipe inside	86.4 × 43.2 ± 0.5			
pipe length, back wall to flare	115 ± 2			
probe centre from back wall	43.7 ± 0.5			
probe length inside	28 ± 0.5			
every seam, piece to piece	under 0.5 Ω			
connector body to copper	under 0.5 Ω			
connector centre pin to copper	open			


Gate. all three horns pass every line. The two that come out closest to each other are the receive horns; the third is the transmitter.

Card gauges for the collar (full size)

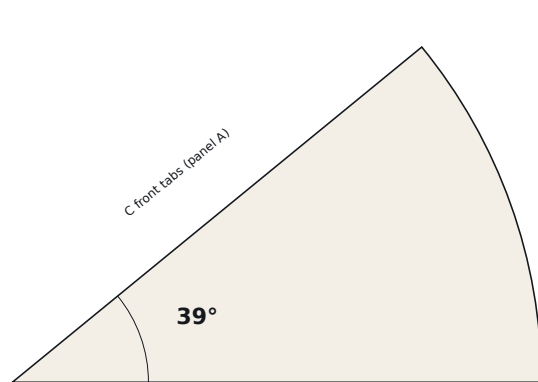Trace onto card and cut out. Lay the long edge along the pipe wall; the slanted edge is where the front tab should be.



lay this edge along the pipe wall

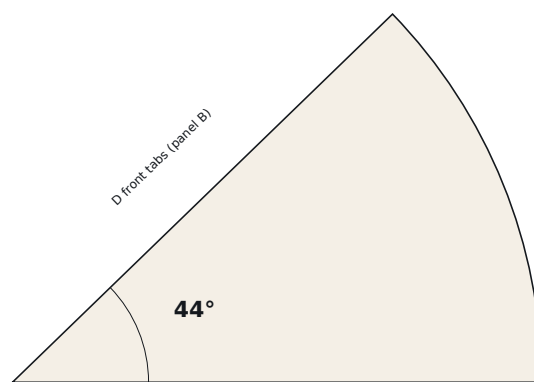

lay this edge along the pipe wall

3 Stage 3: the frame

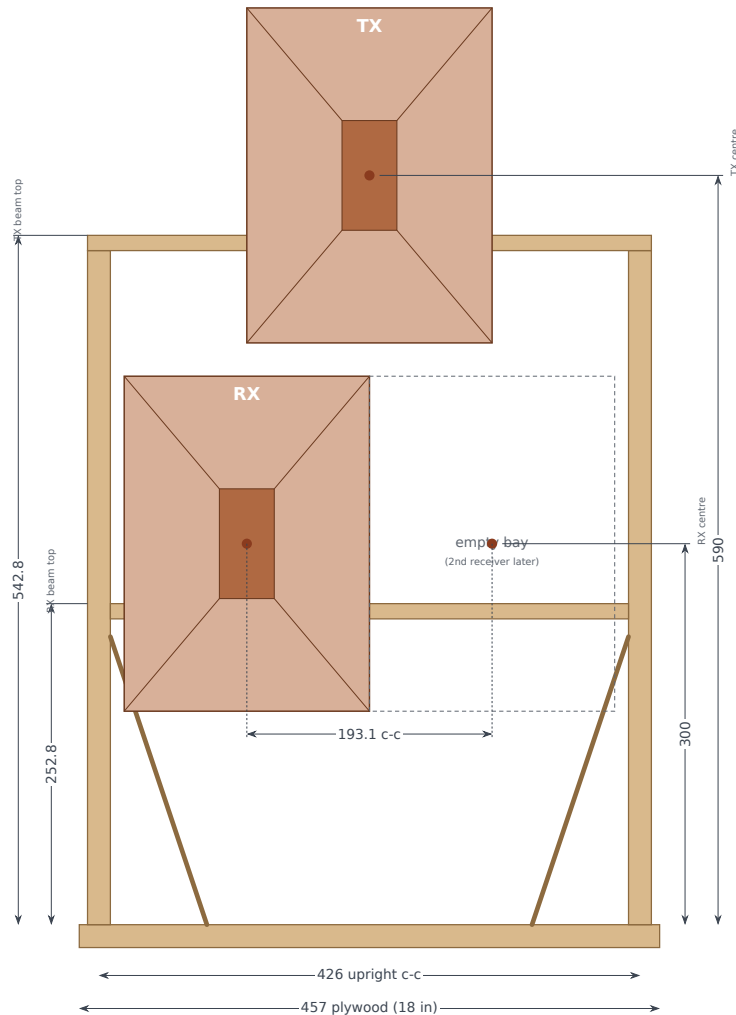


Figure 4: The frame from behind, from where you sit, with the horns in place (drawing from part 1, reduced).

9 Cut and mark

1. Cut the parts on the cut list in part 1: two uprights 530.8, the TX beam 444, the RX beam 408, two braces about 242.2 (leave them long; cut to fit at step 4).
2. On the plywood, draw the centre line front to back, and a line across 145.5 from the front edge. That is the frame line: the centre of both uprights sits on it, 213 either side of the centre line (426 apart).
3. On each upright, mark the top of the RX beam at 252.8 from the foot.

10 Stand the uprights

1. Screw an L-bracket to the front face and another to the back face of each upright foot, flush with the end.
2. Stand each upright on its mark and screw the brackets to the board. Check it is square to the board in both directions with a square, before the last screws go in.

11 Fit the beams

1. **RX beam:** cut a spacer stick exactly 240.8 long. Stand it beside each upright to hold the beam at the right height while you fit it. The beam goes *between* the uprights; drill a 3.5 mm hole through each upright at the beam's centre, and drive a screw through it into a pilot hole in the beam's end.
2. **TX beam:** sits on top of both uprights, its ends flush with their outside faces. Drill 3.5 mm through the beam 426 apart, centred, and screw down into pilot holes in the upright tops.

Check. both beam tops are level, the RX beam top is 252.8 above the board and the TX beam top 542.8. The two diagonals of the frame (foot of one upright to the top of the other) are equal within 2 mm.

12 Braces, saddles and the screen

1. Hold each brace against the inside of its upright, top end 226.8 above the board, foot on the board 128 from the centre line. Mark both ends, cut them, and screw them in.
2. Screw the saddles to the beams: on the RX beam two of them, centred 96.55 either side of the centre line (193.1 apart); on the TX beam one, on the centre line. The U openings face up and run front to back.
3. Make the foil screen: card 293.1×130 , foil on one side. Stand it 50 mm behind the frame, centred, foil towards the horns.

Gate. the frame does not rock on the bench, the saddle centres are where the drawing says, and a horn pipe drops into each saddle without forcing.


4 Stage 4: the breadboard

Seventeen steps. Each adds a handful of parts, ends with something you can measure, and has a picture of the board as it should look afterwards. Power first so later stages have something to run on, then the op-amps, then the signal left to right, then the logic. Nothing is soldered; everything pushes in.

Reading the hole names

Columns 1–63 run left to right; rows a–e are the top bank, f–j the bottom. The five holes of one column in one bank are joined. b14 is row b, column 14. TR-@12 is the **top blue** rail nearest column 12. The rails: top red 5 V, top blue GND, bottom red VANA (12 V analogue), bottom blue GND. Wire colours follow the colour code in part 1.

B1 Rails, bridged and tied

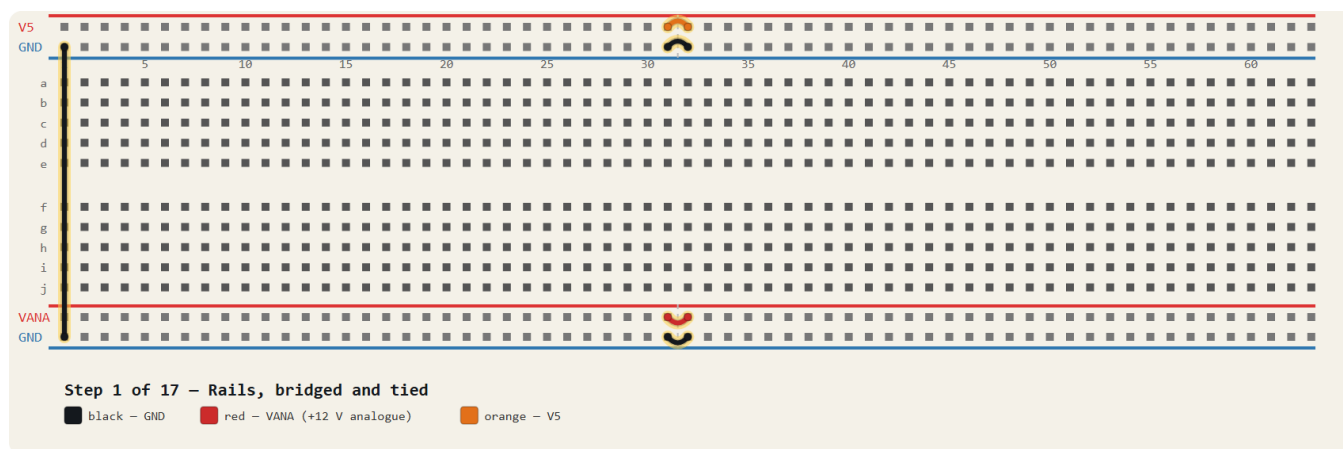


Nothing works until the four rails carry what they claim. Many 830-point boards split every rail at the middle, so the right-hand half of each is dead until you bridge it — and a split you did not notice is the classic reason half a board is unpowered. The last wire ties the two GND rails into one ground.

wire	colour	from → to	what it does
1	orange	TR+@31 → TR+@32	rail bridge (omit if your rails are continuous)
2	black	TR-@31 → TR-@32	rail bridge
3	red	BR+@31 → BR+@32	rail bridge
4	black	BR-@31 → BR-@32	rail bridge
5	black	TR-@1 → BR-@1	tie the two GND rails together

Check. Continuity from each rail's far left hole to its far right hole. If your board's rails are continuous, these four bridges are harmless.

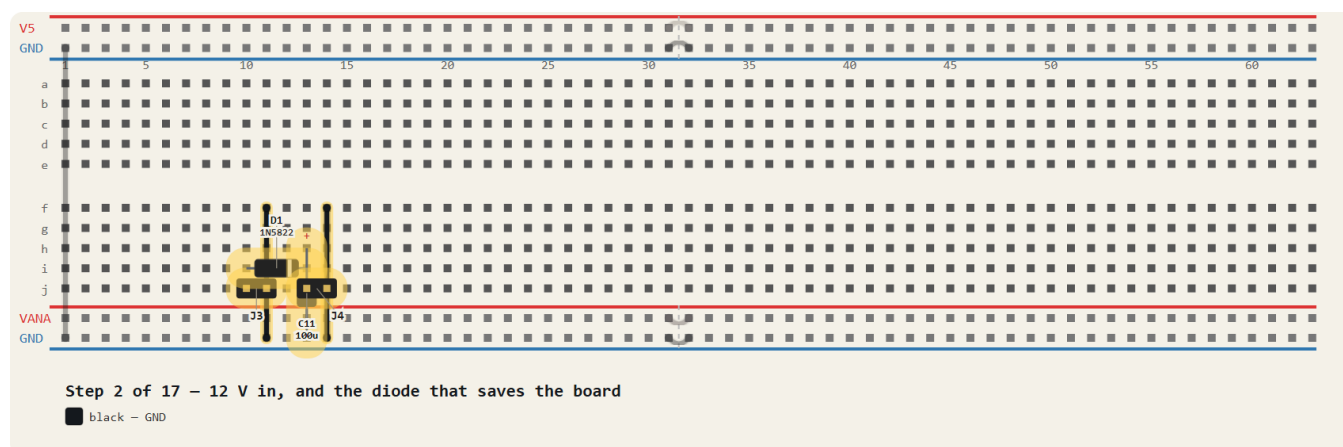B2 12 V in, and the diode that saves the board




J3 takes the 12 V supply. D1 is a series Schottky: get the supply backwards and it simply does not conduct, instead of taking the op-amps and the electrolytics with it. The band on the diode body is the cathode and it faces RIGHT, toward column 13. C11 is the bulk reservoir on the protected side.

part	value	push it in at
J3	12V IN	1→ j10 , 2→ j11
D1	1N5822	A→ i10 , K→ i13
C11	100u	1→ h13 , 2→ BR-@13
J4	TO BUCK IN	1→ j13 , 2→ j14

wire	colour	from → to	what it does
1	black	f11 → BR-@11	J3 GND
2	black	f14 → BR-@14	J4 GND

Check. D1's band toward column 13. C11's + leg toward column 13, its - to the GND rail.

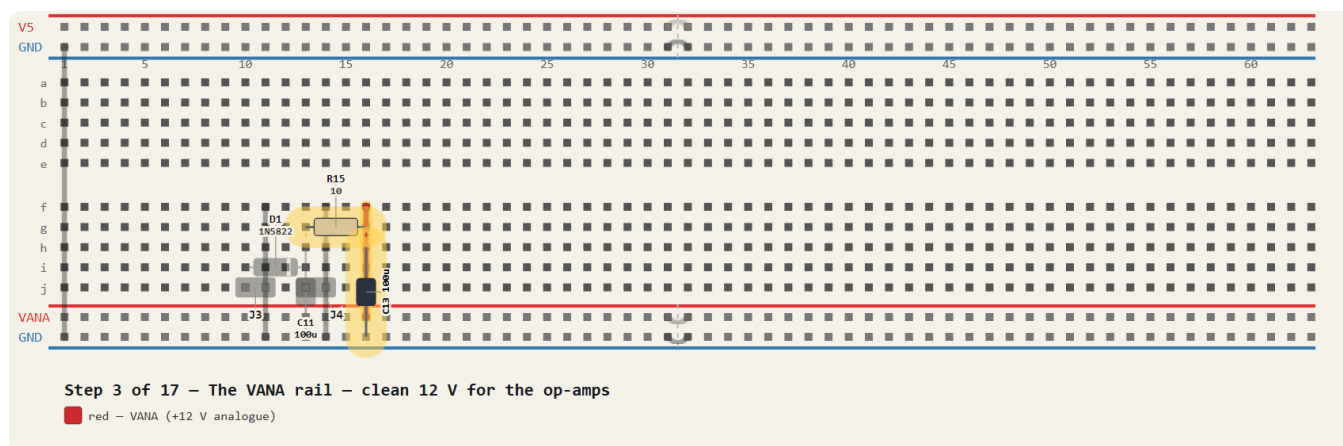B3 The VANA rail — clean 12 V for the op-amps




R15 and C13 are an RC filter, not a resistor someone forgot to remove: 10 ohms into 100 uF rolls off at about 160 Hz, which keeps supply noise out of an amplifier whose whole job is a signal down at 20 mV. The output of that filter is what feeds the bottom red rail.

part	value	push it in at
R15	10	1→g13, 2→g16
C13	100u	1→h16, 2→BR-@16

wire	colour	from → to	what it does
1	red	f16 → BR+@16	VANA node (R15/C13) feeds the bottom red rail

Check. Bottom red rail now sits at 12 V minus the diode drop, about 11.6 V.

B4 5 V in from the buck converter

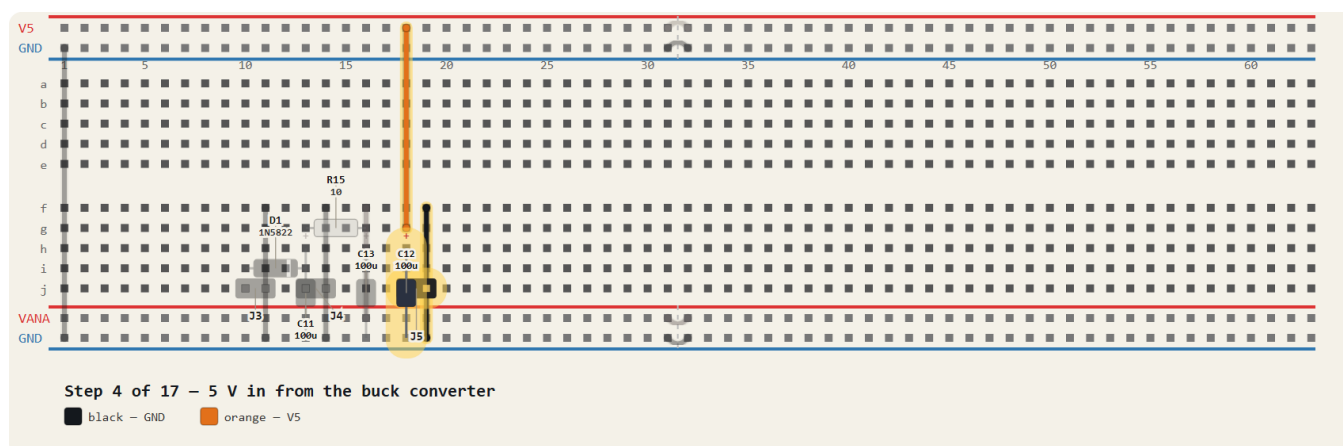


J5 brings 5 V back from the LM2596 after you have set it with nothing else connected. C12 decouples it and the orange wire carries it up to the top red rail, which is what the three RF modules will feed from.

part	value	push it in at
J5	FROM BUCK 5V	1→j18, 2→j19
C12	100u	1→h18, 2→BR-@18

wire	colour	from → to	what it does
1	black	f19 → BR-@19	J5 GND
2	orange	g18 → TR+@18	V5 (J5/C12, bottom col 18) up to the top red rail

Check. Set the buck to 5.00 V BEFORE this wire goes in. Top red rail = 5.00 V.

B5 Seat the two op-amps

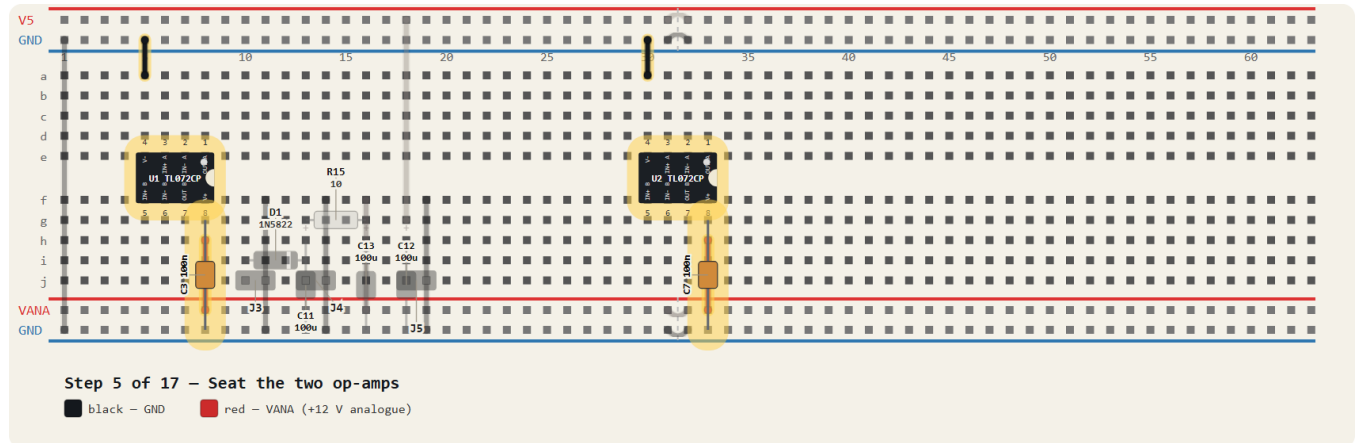


U1 is the two gain stages, U2 the reference buffer and the output. Both straddle the centre channel so the two sides of the package land on separate strips. The notch and the pin-1 dot face RIGHT, toward the higher column. C3 and C7 are the 100 nF decouplers and they go right at pin 8 of each chip, not somewhere tidier.

part	value	push it in at
U1	TL072CP	4→e5, 3→e6, 2→e7, 1→e8, 5→f5, 6→f6, 7→f7, 8→f8
U2	TL072CP	4→e30, 3→e31, 2→e32, 1→e33, 5→f30, 6→f31, 7→f32, 8→f33
C3	100n	1→g8, 2→BR-@8
C7	100n	1→g33, 2→BR-@33

wire	colour	from → to	what it does
1	black	a5 → TR-@5	U1 pin 4 (V-, top col 5) to the GND rail
2	black	a30 → TR-@30	U2 pin 4 (V-, top col 30) to the GND rail
3	red	h8 → BR+@8	U1 pin 8 (V+, bottom col 8) to the VANA rail
4	red	h33 → BR+@33	U2 pin 8 (V+, bottom col 33) to the VANA rail

Check. Pin 1 at e8 (U1) and e33 (U2). Power the board: both chips should sit at room temperature. A warm op-amp means V+ and V- are swapped.

B6 The half-rail reference

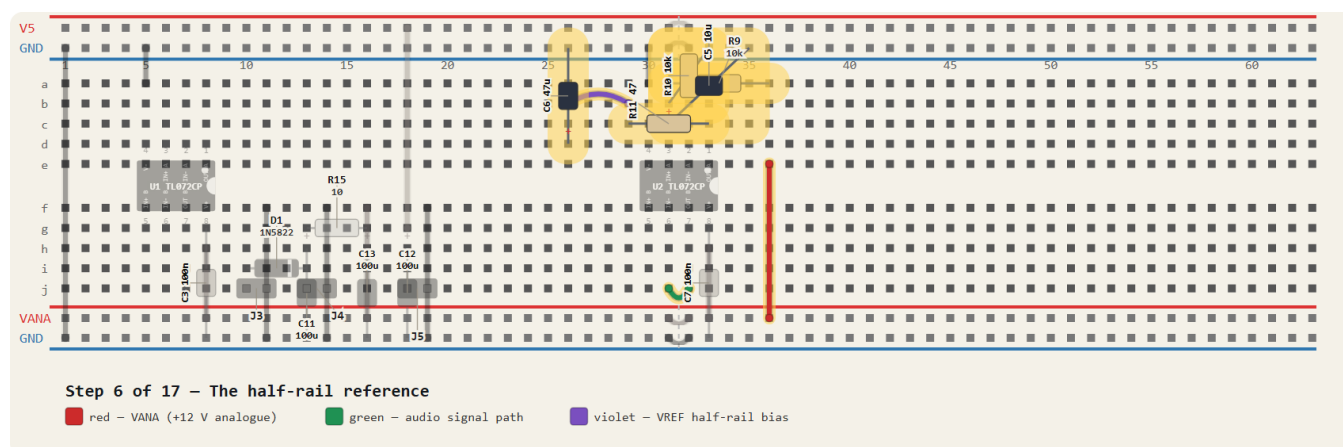

This amplifier runs on a single supply, so 'zero' has to be manufactured: R9 and R10 divide VANA in half at column 31, C5 holds it still, and U2's second half buffers it so the divider is not loaded by everything downstream. R11 and C6 carry that buffered VREF to the node the whole signal chain hangs off.


part	value	push it in at
R9	10k	1→a36, 2→a31
R10	10k	1→b31, 2→TR-@33
C5	10u	1→c31, 2→TR-@35
R11	47	1→c33, 2→c29
C6	47u	1→d26, 2→TR-@26

wire	colour	from → to	what it does
1	red	e36 → BR+@36	R9's VANA end (top col 36) down to the VANA rail
2	green	j32 → j31	U2 pin 7 (col 32) to pin 6 (col 31): unity-gain buffer
3	green	a33 → a32	U2 pin 1 (col 33) to pin 2 (col 32): VREF buffer, unity gain
4	violet	b29 → b26	R11's far end (col 29) to the VREF node (col 26)

Check. VREF (column 26) should read half of VANA, about 5.8 V, and be steady.

B7

Spread VREF along the board

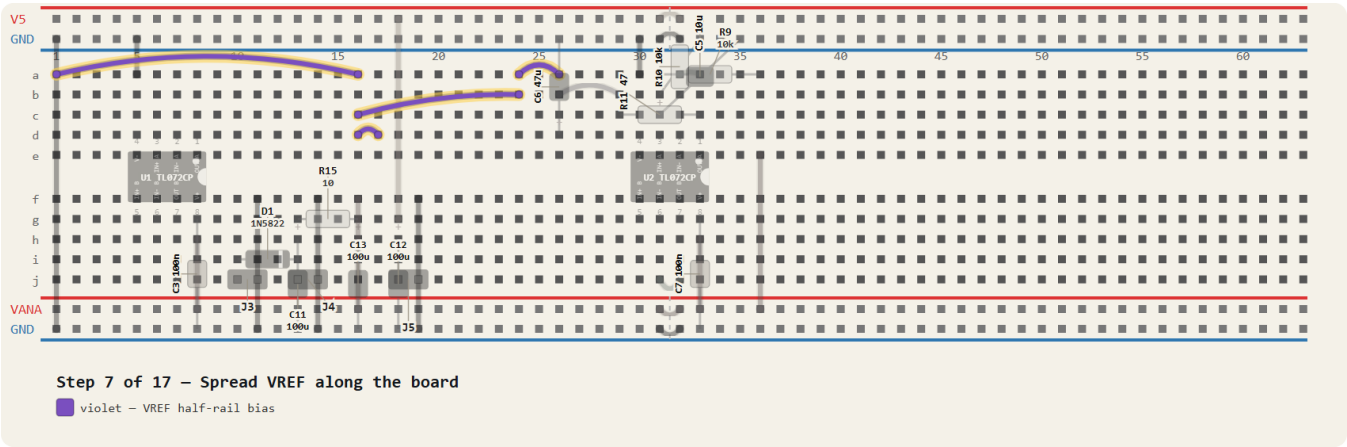


Four violet wires, and they are the reason the amplifier has a zero to swing about. The long one runs the length of row a to reach the input stage at column 1. Do them as a set so none is forgotten — a stage whose VREF is missing is not dead, it is railed, which is a more confusing symptom.

wire	colour	from → to	what it does
1	violet	a26 → a24	VREF -> C9's VREF end
2	violet	b24 → c16	VREF -> R6's VREF end (col 16)
3	violet	d16 → d17	VREF (col 16) -> R4's VREF end (col 17)
4	violet	a1 → a16	VREF -> R2's VREF end (col 1): long run along row a

Check. Every violet wire end reads the same 5.8 V.

B8 The input: mixer IF, terminated

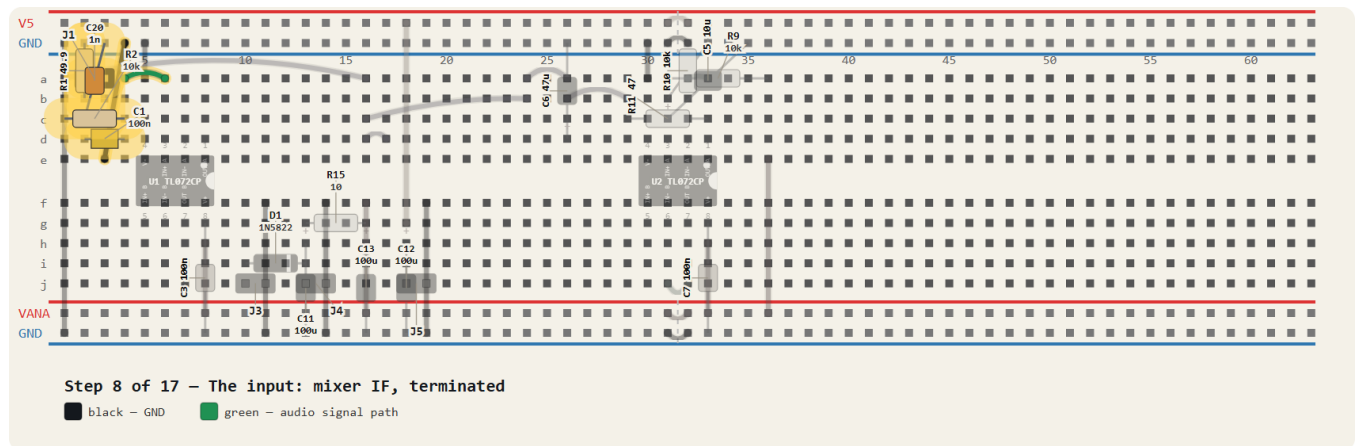


R1 is the 49.9 ohm load the mixer's IF port wants; without it the conversion loss and the flatness wander. C20 shunts the LO that leaks out of that same port at 2.4 GHz, which a TL072 would otherwise rectify into a DC offset. C1 and R2 are the first high-pass, and they are what stop the TX leakage tone from saturating the gain.

part	value	push it in at
J1	MIXER IF	1→a2, 2→a3
R1	49.9	1→b2, 2→TR-@2
C20	1n	1→c2, 2→TR-@3
C1	100n	1→d2, 2→d4
R2	10k	1→c4, 2→c1

wire	colour	from → to	what it does
1	black	e3 → TR-@4	J1 GND
2	green	a4 → a6	AP (C1/R2 node) into U1 pin 3 (IN+ A, col 6)

Check. R1 across the IF input reads 49.9 ohms to ground.

B9 Gain stage A, times 101

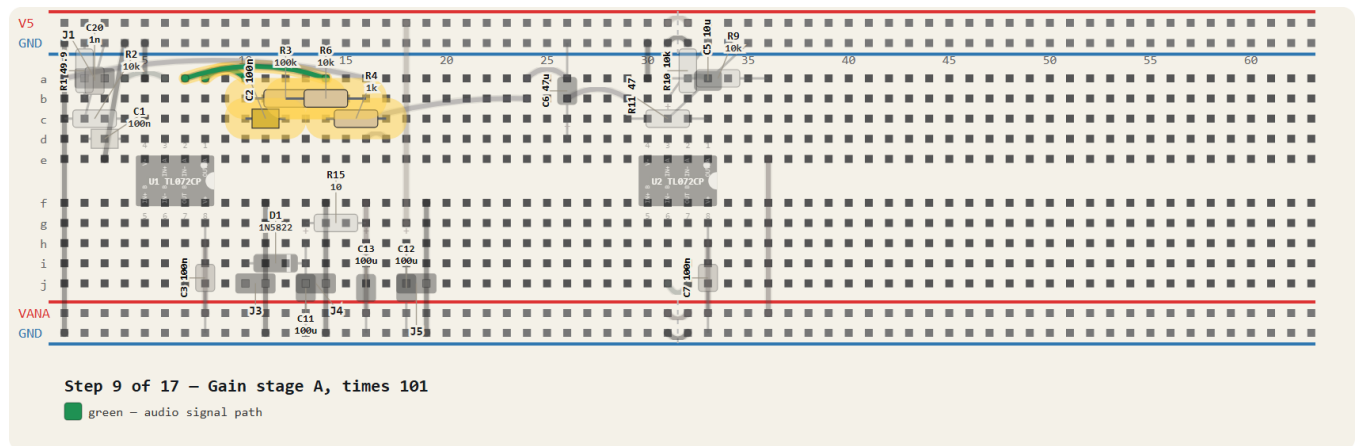

R3 over R4 sets the gain. R4 is 1k for the full 40 dB, but fit 4.7k on first power-up for a gain of 22: if the TX leakage is stronger than you expected, a lower first gain is the difference between seeing it and clipping on it. C2 and R6 are the second high-pass into stage B.


part	value	push it in at
R3	100k	1→b14, 2→b10
C2	100n	1→c10, 2→c12
R4	1k	1→c14, 2→c17
R6	10k	1→b12, 2→b16

wire	colour	from → to	what it does
1	green	a8 → a10	U1 pin 1 (OUT A, col 8) to the AOUT node (col 10)
2	green	a14 → a7	AM node (R3/R4) back to U1 pin 2 (IN- A, col 7)

Check. Inject 10 mV at 1 kHz: about 107 mV out of stage A with R4 at 4.7k.

B10

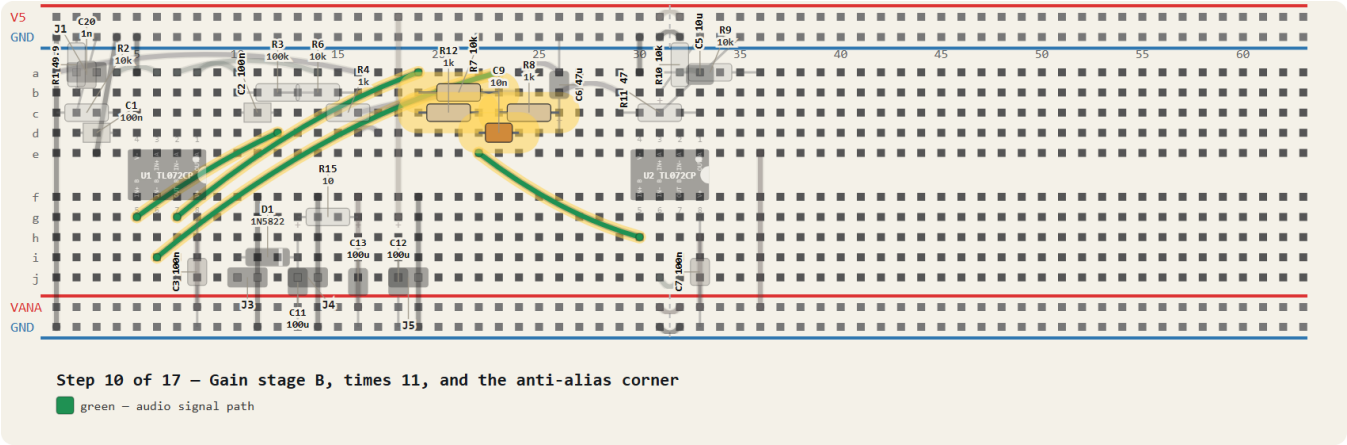Gain stage B, times 11, and the anti-alias corner



R7 over R8 gives the second 21 dB. R12 with C9 is the 15.9 kHz low-pass that limits the noise bandwidth reaching the sound card. The last wire takes that filtered node across the channel into U2’s spare half.


part	value	push it in at
R7	10k	1→b23, 2→b19
R8	1k	1→c23, 2→c26
R12	1k	1→c19, 2→c22
C9	10n	1→d22, 2→d24

wire	colour	from → to	what it does
1	green	d12 → g5	BP (C2/R6 node) across the channel into U1 pin 5 (IN+ B, bottom col 5)
2	green	g7 → a19	U1 pin 7 (OUT B, bottom col 7) up to the BOUT node (col 19)
3	green	a23 → i6	BM node (R7/R8) across to U1 pin 6 (IN- B, bottom col 6)
4	green	e22 → h30	LP (R12/C9 node) across to U2 pin 5 (IN+ B, bottom col 30)

Check. Total gain now about 61 dB. Sweep it: -3 dB at 15.9 kHz, -6 dB at 159 Hz.

B11

Output, isolated and bled to ground

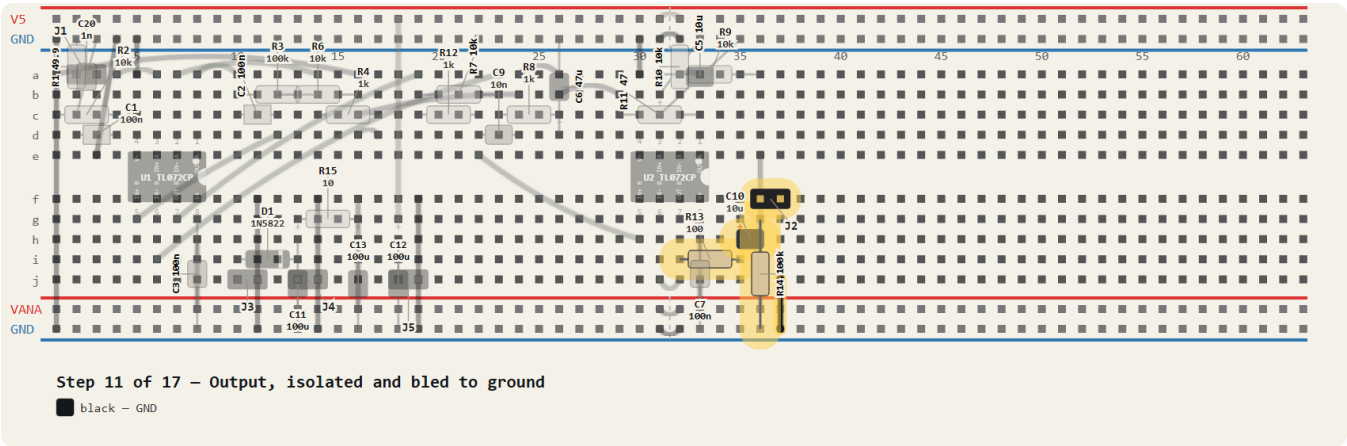

R13 and C10 hand the signal to the sound card through a series resistor, so a cable capacitance does not hang directly off an op-amp output. R14 bleeds the coupling cap so the jack is not left holding a charge, and J2 is the audio-left output to the interface.


part	value	push it in at
R13	100	1→i32, 2→i35
C10	10u	1→h35, 2→h36
R14	100k	1→g36, 2→BR-@36
J2	AUDIO L	1→f36, 2→f37

wire	colour	from → to	what it does
1	black	j37 → BR-@37	J2 GND

Check. Output DC near 0 V after C10. Finger on the input gives a hum: the amp is alive.

B12

Three 5 V feeds for the RF modules

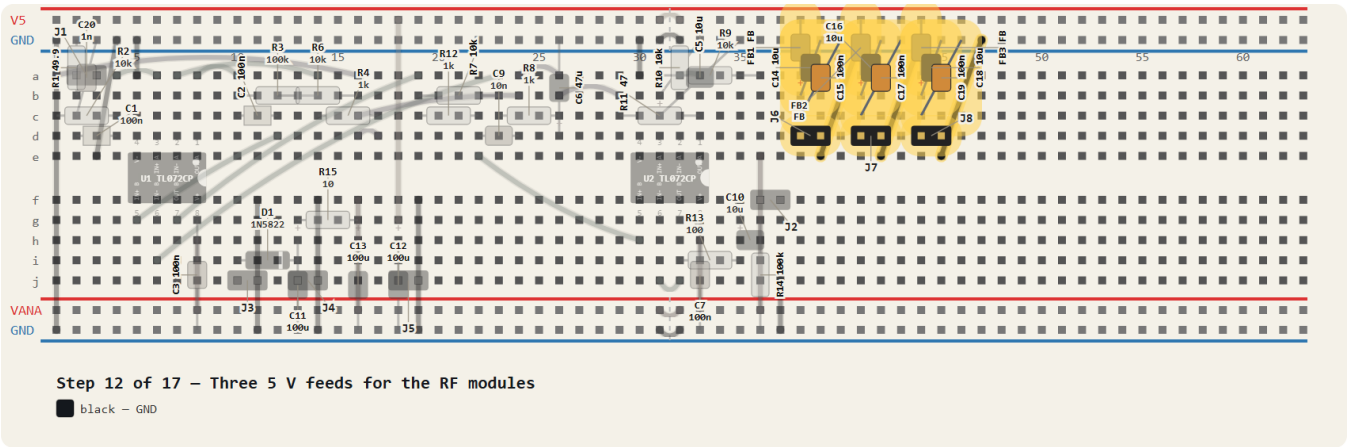


The ADF4351, the PA and the LNA each get a ferrite bead and their own 10 uF plus 100 nF pair, so one module’s switching noise does not arrive at the next one along the rail. Identical blocks at columns 38, 41 and 44 — build one, check it, then repeat it twice.

part	value	push it in at
FB1	FB	1→TR+@38, 2→a38
C14	10u	1→b38, 2→TR-@39
C15	100n	1→c38, 2→TR-@40
J6	ADF4351 5V	1→d38, 2→d39
FB2	FB	1→TR+@41, 2→a41
C16	10u	1→b41, 2→TR-@42
C17	100n	1→c41, 2→TR-@43
J7	PA 5V	1→d41, 2→d42
FB3	FB	1→TR+@44, 2→a44
C18	10u	1→b44, 2→TR-@45
C19	100n	1→c44, 2→TR-@46
J8	LNA 5V	1→d44, 2→d45

wire	colour	from → to	what it does
1	black	e39 → TR-@41	J6 GND
2	black	e42 → TR-@44	J7 GND
3	black	e45 → TR-@47	J8 GND

Check. 5.00 V at all three of J6, J7, J8 with nothing plugged into them.

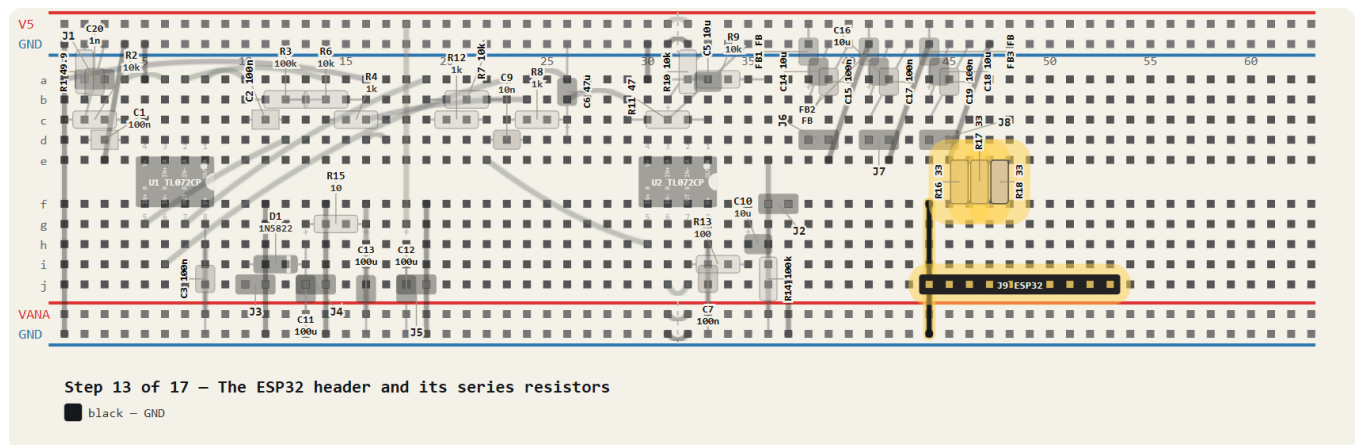B13 The ESP32 header and its series resistors




J9 is where the radar's ESP32 lands. R16 to R18 are 33 ohm series resistors on SCK, MOSI and LE: they damp the edges so a 2.54 mm breadboard run does not ring into the PLL's logic inputs. Each one hops the centre channel into the top bank.

part	value	push it in at
J9	ESP32	1→j44, 2→j45, 3→j46, 4→j47, 5→j48, 6→j49, 7→j50, 8→j51, 9→j52, 10→j53
R16	33	1→f45, 2→e46
R17	33	1→f46, 2→e47
R18	33	1→f47, 2→e48

wire	colour	from → to	what it does
1	black	f44 → BR-@44	J9 pin 1 GND

Check. Each resistor reads 33 ohms between its two strips, and nothing else.

B14 SPI across to the ADF4351

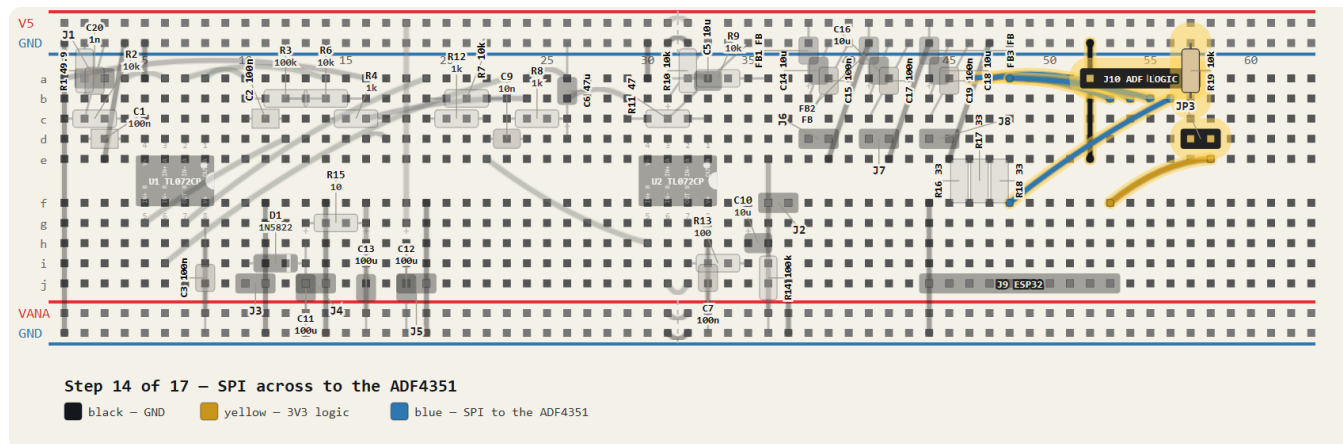


Four blue wires carry the damped SPI and the lock-detect line up to J10. R19 pulls CE down so the synthesiser's output stays OFF until something deliberately enables it, and JP3 is the link that enables it. The yellow wire brings 3V3 over from the ESP32 — the ADF4351 board is 3.3 V logic and needs no level shifting.

part	value	push it in at
J10	ADF LOGIC	1→a52, 2→a53, 3→a54, 4→a55, 5→a56, 6→a57
R19	10k	1→b57, 2→TR-@57
JP3	CE EN	1→d57, 2→d58

wire	colour	from → to	what it does
1	black	e52 → TR-@52	J10 pin 1 GND
2	blue	a46 → b53	R16 out (top col 46) -> J10 pin 2 SCK_O (col 53)
3	blue	a47 → b54	R17 out (top col 47) -> J10 pin 3 MOSI_O (col 54)
4	blue	a48 → b55	R18 out (top col 48) -> J10 pin 4 LE_O (col 55)
5	blue	f48 → b56	J9 pin 5 LD (bottom col 48) -> J10 pin 5 LD (top col 56)
6	yellow	f53 → e58	J9 pin 10 3V3 (bottom col 53) -> JP3 pin 2 (top col 58)

Check. With JP3 off, CE reads 0 V. The radar must boot with RF off.

B15 The A4988 stepper header

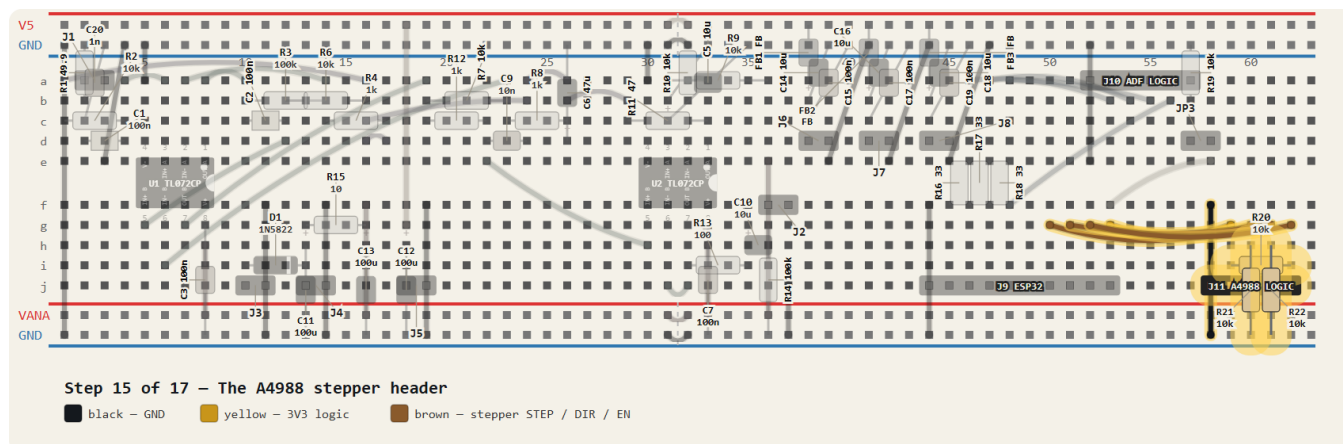

Only for the optional turntable; skip the whole step if you are not fitting one. R20 pulls EN up so the driver is disabled until the ESP32 says otherwise, and R21 and R22 pull STEP and DIR down so a floating input cannot make the motor twitch at power-up. The three brown wires are the control lines.


part	value	push it in at
J11	A4988 LOGIC	1→j58, 2→j59, 3→j60, 4→j61, 5→j62
R20	10k	1→i59, 2→i62
R21	10k	1→h60, 2→BR-@60
R22	10k	1→h61, 2→BR-@61

wire	colour	from → to	what it does
1	black	f58 → BR-@58	J11 pin 1 GND
2	yellow	g53 → g59	3V3 -> J11 pin 2 / R20 (bottom col 59)
3	brown	g50 → g60	J9 pin 7 STEP (col 50) -> J11 pin 3 (col 60)
4	brown	g51 → g61	J9 pin 8 DIR (col 51) -> J11 pin 4 (col 61)
5	brown	g52 → g62	J9 pin 9 EN (col 52) -> J11 pin 5 (col 62)

Check. EN sits at 3V3, STEP and DIR at 0 V, with the ESP32 unplugged.

B16

The SYNC divider back to the sound card

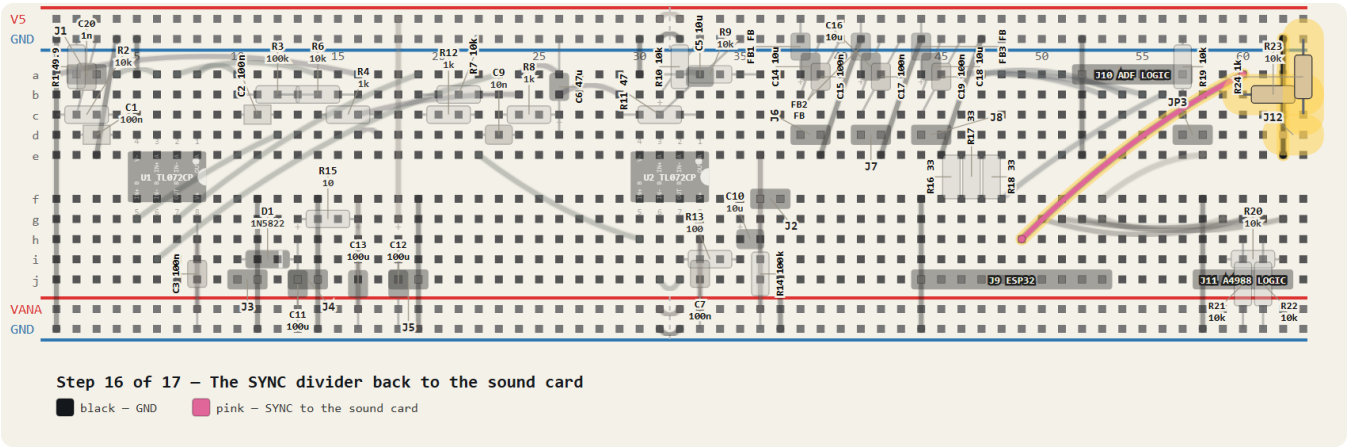


The last block, and the one that makes the whole radar measurable: R23 and R24 divide the ESP32’s 3.3 V chirp marker down to about 0.3 V, which is a line-level signal the sound card’s sync input (INPUT 2) can take. Without it the laptop cannot cut the beat signal into chirps and there is no range axis at all.

part	value	push it in at
R23	10k	1→b60, 2→b63
R24	1k	1→c63, 2→TR-@63
J12	AUDIO R	1→d63, 2→d62

wire	colour	from → to	what it does
1	black	e62 → TR-@62	J12 GND
2	pink	h49 → a60	J9 pin 6 SYNC (bottom col 49) up to R23 (top col 60)

Check. A 135 Hz square wave of about 0.3 V at J12 once radar_ctl is running.

B17 Before you power anything

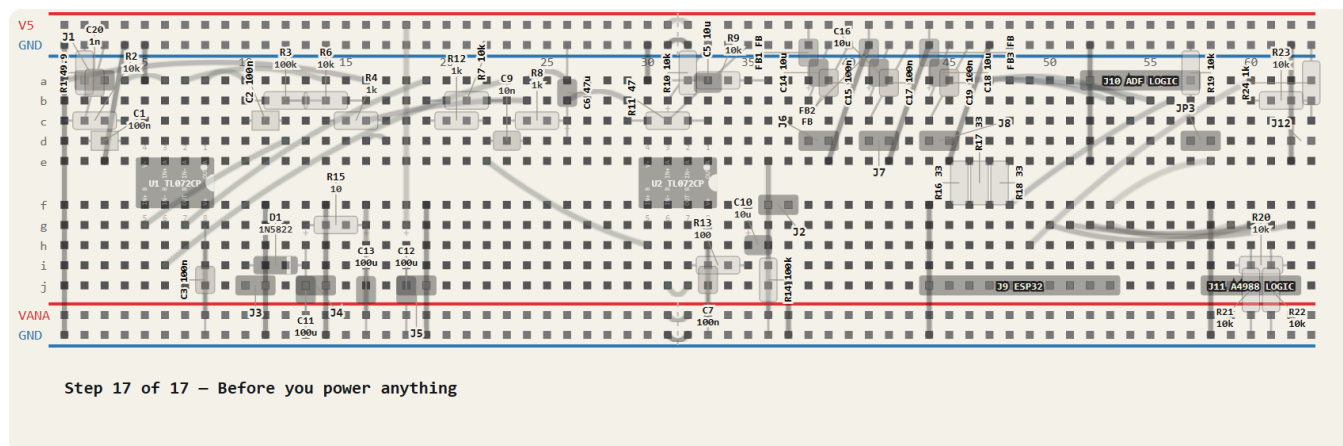

The board is finished. These are the measurements that catch a build error while it is still cheap, with the supply DISCONNECTED and nothing plugged into the headers.

Check. Ohm-meter, all with power off: GND to VANA, GND to V5 and GND to 3V3 must each read open (over 1 kohm). Any of them near zero is a short — find it before you connect 12 V. Then work the test blocks in breadboard/multisim/.

Gate. step B17's resistance checks pass, with the 12 V supply disconnected.

5 Stage 5: power

Set the buck converter before it touches anything

The LM2596 board arrives set to anything up to 12 V out. Fed straight into the ADF4351 or an amplifier, that is an expensive few seconds. Set it to 5.00 V first, with nothing on its output.

13 Set the buck converter to 5.00 V

1. Wire J4 (pins 1 +, 2 –) to the buck's IN+ and IN–. Leave J5 and J6–J8 empty.
2. Plug the 12 V supply into J3. Put the meter on the buck's OUT+ and OUT–.
3. Turn the small brass screw on the blue trimmer until the meter reads 5.00 V. It is many turns end to end; be patient.
4. Unplug the supply. Wire the buck's OUT+ and OUT– to J5.

14 Measure the rails

Plug the 12 V supply back in, with still nothing on J1, J2, J6–J12.

rail	measure between	expect	if not
VPROT	D1 cathode (col 13) and GND	11.6–11.8 V	0 V: D1 backwards or the supply plug is wired backwards
VANA	bottom red rail and GND	11.5–11.8 V	low: R15 wrong value, or a short loading it
VREF	violet node (col 26) and GND	half of VANA, about 5.8 V	0 or VANA: R9/R10 or U2 pin 1/3 wiring
5 V	top red rail and GND	5.00 V	re-set the buck
J6, J7, J8	pin 1 to pin 2	5.00 V each	0 V: ferrite bead not in the column

15 Connect the modules one at a time

Supply off. Connect J6 to the ADF4351's 5 V and GND pins, supply on, check it still reads 5 V and the supply is not straining; supply off. Repeat with J7 to the PA and J8 to the LNA. Use red and black 22 AWG twisted together, as short as reaches.

Gate. every rail in the table reads right, and all three modules powered together still leave 4.9–5.0 V at their headers.

6 Stage 6: firmware and software

The firmware (radar_ctl) and the laptop software (ground_station) are in the repository's history rather than on this branch. Get a copy of both once:

Getting the code

```
git archive 3f95c6d firmware ground_station | tar -x -C ~/radar-sw
```

That puts firmware/radar_ctl/radar_ctl.ino and the ground_station/ folder in ~/radar-sw.

16 Wire the ESP32 and the PLL's logic

Only the logic, for now: no RF cables, PA and LNA unplugged.

header	breadboard pin	goes to	note
J9 (10 wires)	1 GND	ESP32 GND	
	2 SCK	ESP32 D18	
	3 MOSI	ESP32 D23	
	4 LE	ESP32 D5	
	5 LD	ESP32 D19	lock detect, back to the ESP32
	6 SYNC	ESP32 D25	
	7, 8, 9	ESP32 D26, D27, D14	STEP, DIR, EN: turntable only, may be left off
	10 3V3	ESP32 3V3	
J10 (6 wires)	1 GND, 2 CLK, 3 DATA, 4 LE, 5 LD, 6 CE	ADF4351 header	match by the printed names , not by position: boards differ
JP3		a jumper cap	on = the PLL enabled

17 Flash radar_ctl

1. In the Arduino IDE, install the *esp32* board package (Espressif, 2.x or 3.x) and pick the board **“ESP32 Dev Module”**.
2. Open *radar_ctl.ino*. Check `F_REF_HZ` matches the crystal printed on your ADF4351 board's can: 25 MHz on nearly all of them.
3. Plug the ESP32 into the laptop by USB, pick its port, and upload. If the upload stalls at “Connecting...”, hold the BOOT button until it starts.
4. Open the serial monitor at **115200** baud, line ending “Newline”, and type ?.

Check. the reply is a line of JSON ending in `"lock":1`, with `"rf":0` and `"sweep":0`. The board boots silent: it transmits nothing until you tell it to.

if you see	look at
nothing at all	baud rate 115200; the right port; a charge-only USB cable
"lock":0	F_REF_HZ against the crystal; CLK, DATA and LE swapped at J10; JP3 cap missing (CE low); 5 V at J6

18 Install the laptop software

1. In *ground_station/*: `pip install -r requirements.txt` (Python 3.10 or newer).

2. `python radar_acquire.py --selftest`. It invents a target at 8 m and should find it there. This proves the software before any hardware is involved.
3. Plug in the UMC404HD and run `python -m sounddevice`. Note the number next to the UMC404HD's input: that is `--device N` from now on.

Gate. lock:1 on ?, and the self-test finds its 8 m target.

7 Stage 7: mount and cable

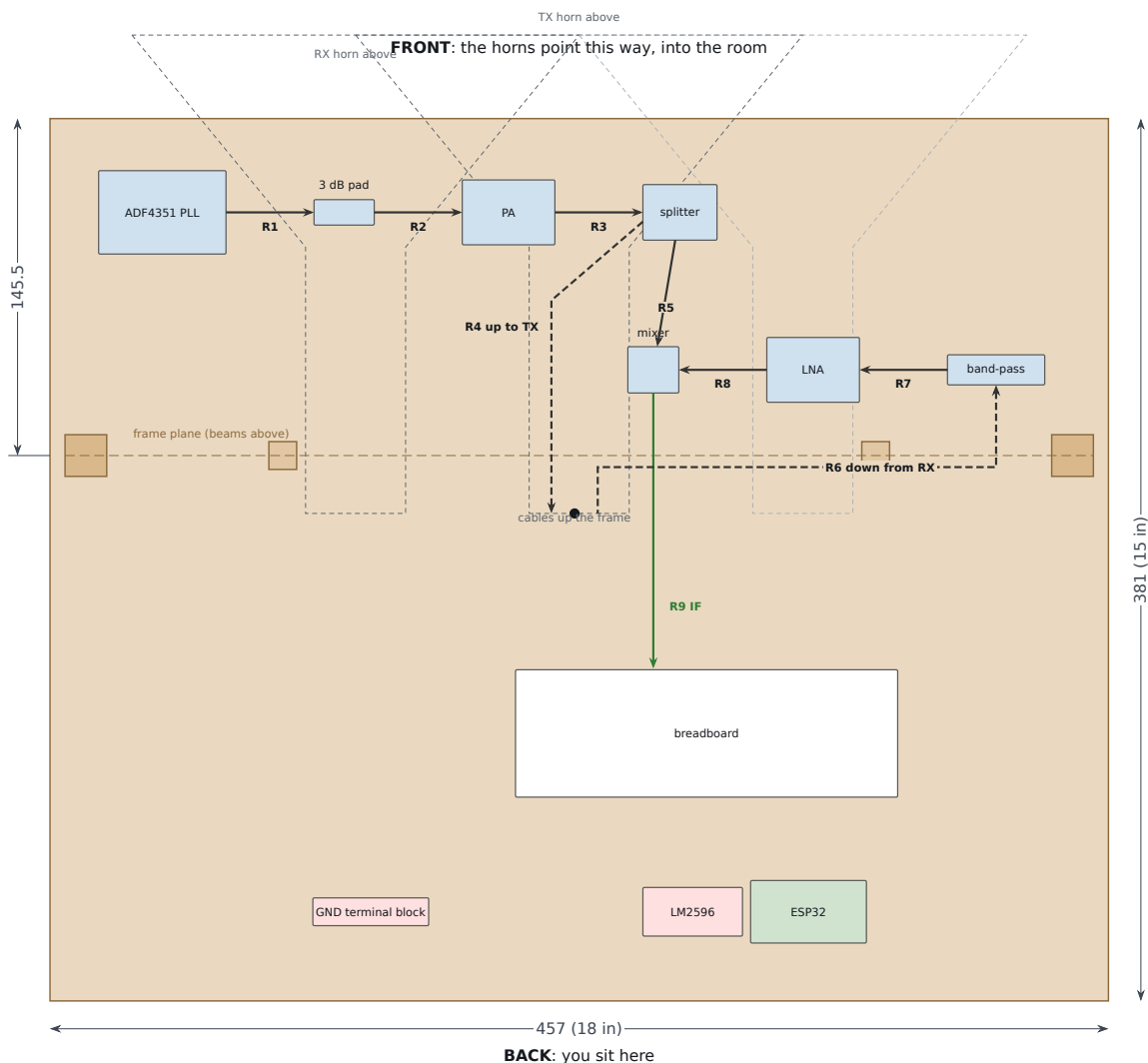


Figure 5: Where everything goes on the board, seen from above (from part 1). Horns at the top, your seat at the bottom.

19 Mount the horns

1. Roll each horn onto its side so the connector points **left**. The pipe's narrow wall now sits on the saddle and the long side of the mouth runs up and down.
2. Drop the pipe into its saddle and slide it until the saddle is 90 behind the throat (where flare meets pipe). Line the saddle cheeks with rubber or foam tape and tighten the two M4 clamp screws just until the horn will not slide.
3. RX horn: the left saddle on the lower beam. TX horn: the saddle on the top beam. The right saddle on the lower beam stays empty for the second receiver.
4. Lay a straightedge across the mouths: all three planes (RX, TX, and where the empty bay's mouth will be) should touch it. Adjust by sliding in the saddles.

Check. RX horn centre 300 above the board, $193.1/2 = 96.6$ left of the centre line; TX horn centre 590 above the board, on the centre line. The mouths overhang the board's front edge by about 36.

20 Lay out the modules

Place the modules where the plan above puts them and fix them with foam tape or small brackets: the transmit chain (ADF4351, pad, PA, splitter) along the front, the receive chain (band-pass, LNA, mixer) behind it, the breadboard behind that. Keep the PA and LNA at least 10 cm apart.

21 The SMA cables

Connect in this order, finger tight, then an eighth of a turn with the spanner. Look into each connector before mating it.

run	from	to	cable
R1	ADF4351 RF OUT A	3 dB pad	20 cm
R2	3 dB pad	PA in	20 cm (or pad straight on)
R3	PA out	splitter input (S)	20 cm
R5	splitter port 2	mixer LO	20 cm
R7	band-pass out	LNA in	20 cm
R8	LNA out	mixer RF	20 cm
R4	splitter port 1	TX horn, up the middle of the frame	1 m, tied every 10 cm
R6	RX horn, down the middle of the frame	band-pass in	60 cm
R9	mixer IF	breadboard J1: centre to pin 1, braid to pin 2	pigtail

22 Audio and the last wires

- J2 (beat) to the UMC404HD **INPUT 1**, J12 (sync) to **INPUT 2**, each with a shielded 1/4 in TS cable: tip to pin 1, sleeve to pin 2.
- On the UMC404HD: 48 V phantom power **off**; both gain knobs low (about 9 o'clock) to start; direct monitor irrelevant.
- In the laptop's sound settings: 44.1 kHz, 16-bit, and every "enhancement", automatic gain and noise suppression turned off.

Why sync goes on INPUT 2, not 3

The stage-1 software records the interface's *first two* inputs: beat, then sync. Plugged into INPUT 3, the sync is never read and the software reports no sync. When the second receiver goes in (stage 2), its beat takes INPUT 2 and the sync moves to INPUT 3, and the software is told to read three channels.

Gate. the whole chain is cabled and every SMA done up, and nothing is powered yet. A finger-tight SMA costs about 1 dB, and you will chase it for an evening once there is a signal to blame it on.

8 Stages 8 to 10: bring-up

Power on in this order: 12 V supply, then the ESP32's USB, then the UMC404HD's USB. Point the horns at an open room, not a wall a metre away.

23 Checkpoint: the transmit power (if you can measure it)

CW 2440 parks the PLL on one frequency with RF on. With a power meter, or an RTL-SDR behind a 30 dB attenuator, at the splitter's port 2 (the LO arm) in place of the mixer: **+10.5 ± 2 dBm**. Type RF0FF and put the cable back. No meter? Skip this: the next check covers the same ground.

24 First light: the leakage tone

Type SWEEP 1. Open any audio recorder (Audacity is fine) on the UMC404HD and watch INPUT 1.

Check. a low tone with a strong part at about 26 Hz. It is the transmitter leaking straight across the short gap into the receive horn, and it proves the PLL, the PA, the splitter, the LO, the LNA, the mixer and the amplifier all work, in one go. Set INPUT 1's gain so this tone peaks well below clipping, then never touch that knob again.

Check. INPUT 2 shows a clean square wave at about 135 Hz (6.4 ms high, 1 ms low), about 0.3 V. That is the sync.

No leakage tone? Work backwards from the mixer

Sync present but no tone: check LO drive first (R5 done up, splitter port 2), then the IF pigtail to J1, then the amplifier (each stage's output should sit at VREF with no signal). No sync either: SWEEP 1 not sent, or J12's wire not at INPUT 2.

25 First measurement: the walk test

In ground_station/, start the console and the acquisition (two terminals):

```
python server.py
python radar_acquire.py --device N --ctl /dev/ttyUSB0 --server http://localhost:8080
```

(on Windows the port is COM3 or similar). Open <http://localhost:8080>. Walk towards the horns from about 5 m.

Check. range counts down as you approach and velocity reads negative, about your walking speed; walk away and it goes positive. Stand still and you vanish: that is not a fault, the radar subtracts everything that is not moving, along with the walls. Wave an arm and you come back.

Gate. stand still at 3, 5 and 8 m from the mouths, measured with a tape, while waving an arm: the printed range is within 0.4 m each time.

26 The measurement that decides it: clutter cancellation

Do this the day the chain first works. Point the radar at a still room with nobody moving. Record one block, then another a few seconds later, and subtract the range profiles. The ratio of the strongest echo to what is left is the clutter cancellation, in dB.

you measure	what it means
over 50 dB	the radar can find a small drone at 10 m indoors: carry on
40–50 dB	marginal at 10 m, fine closer in
around 30 dB	no amount of software will find the drone at 10 m. The fix is mechanical: a rigid mount, more mass, no fan or air currents, nobody walking about

27 The drone link

The drone's control link is on 915 MHz so the radar can have the whole 2.4 GHz band. Before the two are ever on together: with SWEEP 1 running and the beam on the drone (props off), the link quality on the RadioMaster must stay at 100 and its signal strength must not move.

Gate. clutter cancellation over 50 dB, and the drone link unaffected by the sweep. Then fly, keeping the drone moving towards or away at 0.1 m/s or more: a pure hover is subtracted along with the walls.

9 When something is wrong

symptom	likely cause, in order
"lock":0	F_REF_HZ wrong; CLK/DATA/LE swapped at J10 (match the printed names); JP3 cap off; no 5 V at J6
no sync on INPUT 2	SWEEP not on; J12 at the wrong input; R23/R24 not at columns 60 and 63
sync present, no beat tone	LO cable R5; IF pigtail at J1 reversed; mixer RF/LO swapped; PA or LNA not powered
beat tone clips	INPUT 1 gain too high; or R4 is 1 k while something upstream is too strong: fit 4.7 k at R4 (gain 22) to diagnose
a steady hum, 50 or 60 Hz	audio cables not shielded, or the laptop charger: try it on battery; star-ground everything at the terminal block
range reads consistently long or short	--fs not matching the sound card's real rate; a different sweep from the one the software assumes (use --ctl so it reads the sweep back)
a target at a fixed range that never moves	a reflection from the frame or the bench itself; check the foil screen is in place and nothing metal is near the mouths
nothing detected beyond a few metres	horns not facing the same way; RX cable R6 loose; the RX probe bent; clutter cancellation too low (stage 10)
the PA is very hot	normal is warm. Too hot to touch: check its supply is 5 V, not 12

Finished



That is the whole radar: range and radial speed of anything moving in the beam. The empty bay on the lower beam, the spare horn and the spare SPF5189Z are there for the second receiver, which adds direction.